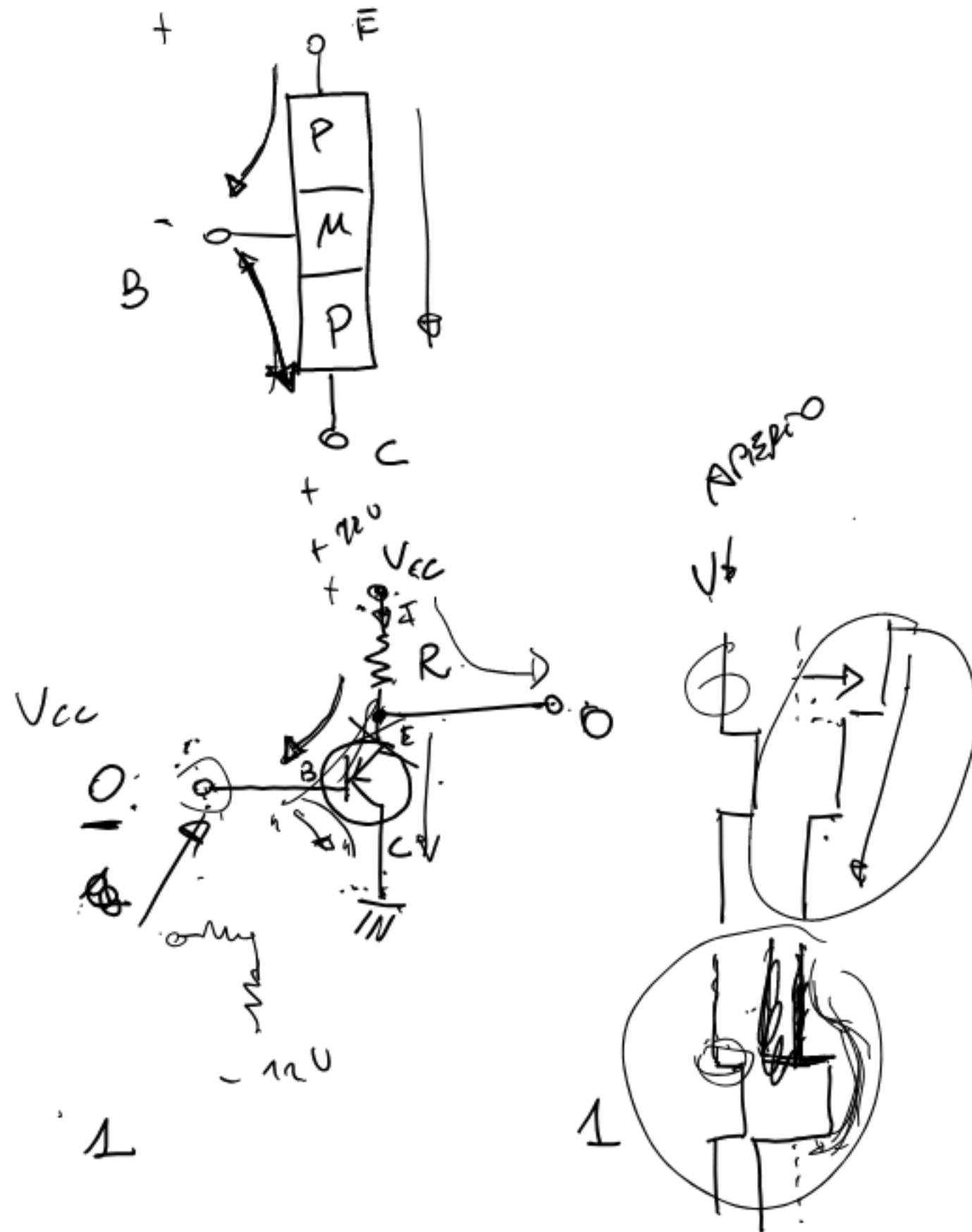




ELETRONICA ANALOGICA

02/04/2020





SONDE (V)

GRAFICO

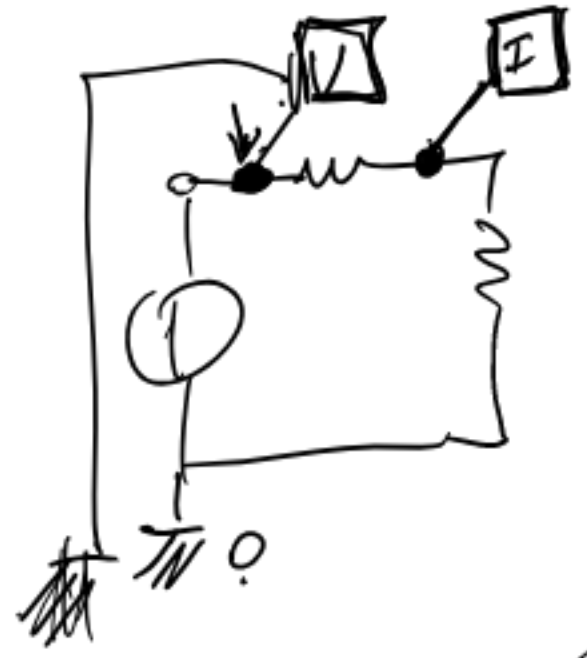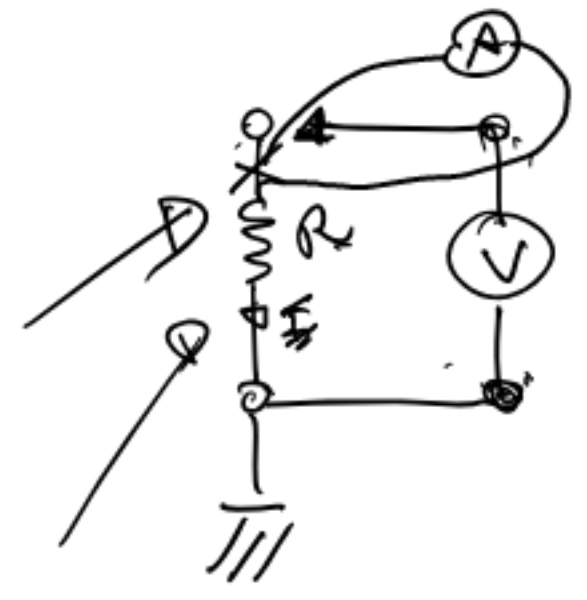

CAMPION / SAMPLE

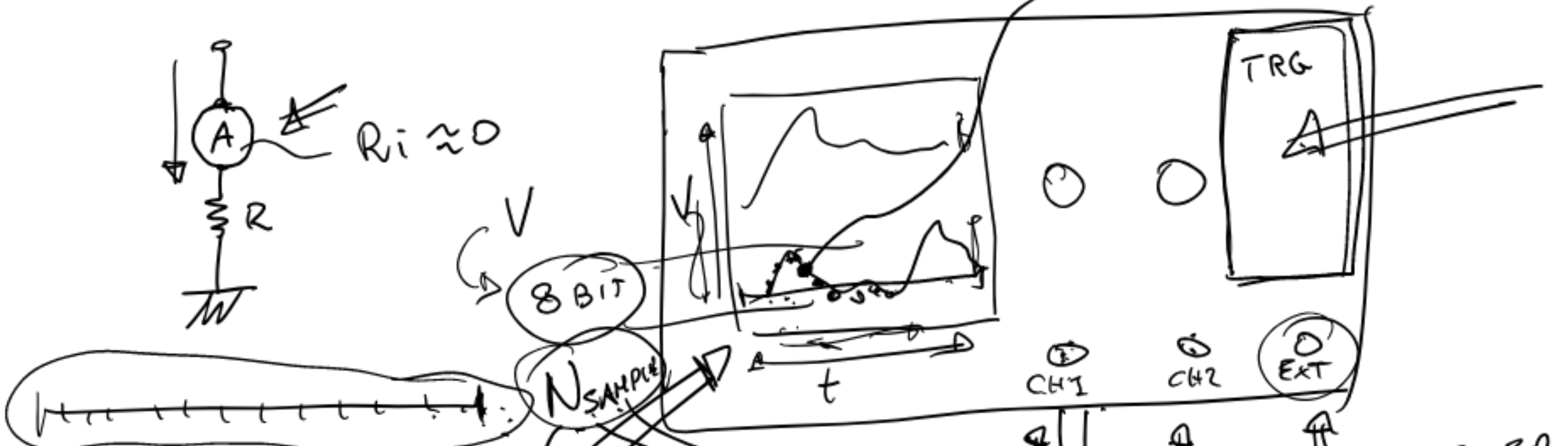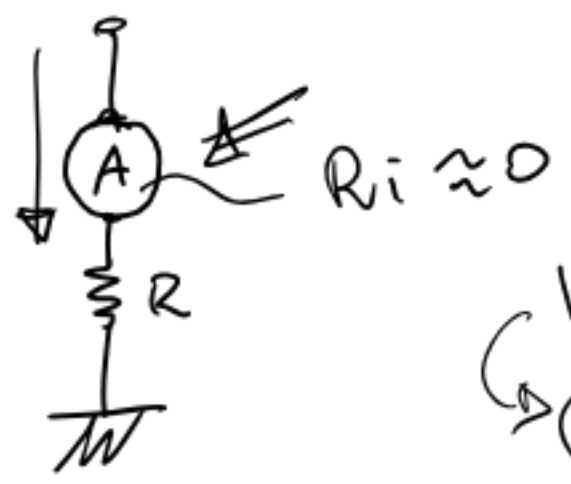

Δt

1ms

20 GHz

$\approx 20 \text{ kE}$





1 GHz

10³ SAMPLES


TRIGGER

TRIGGER

TRIGGER \rightarrow ESS

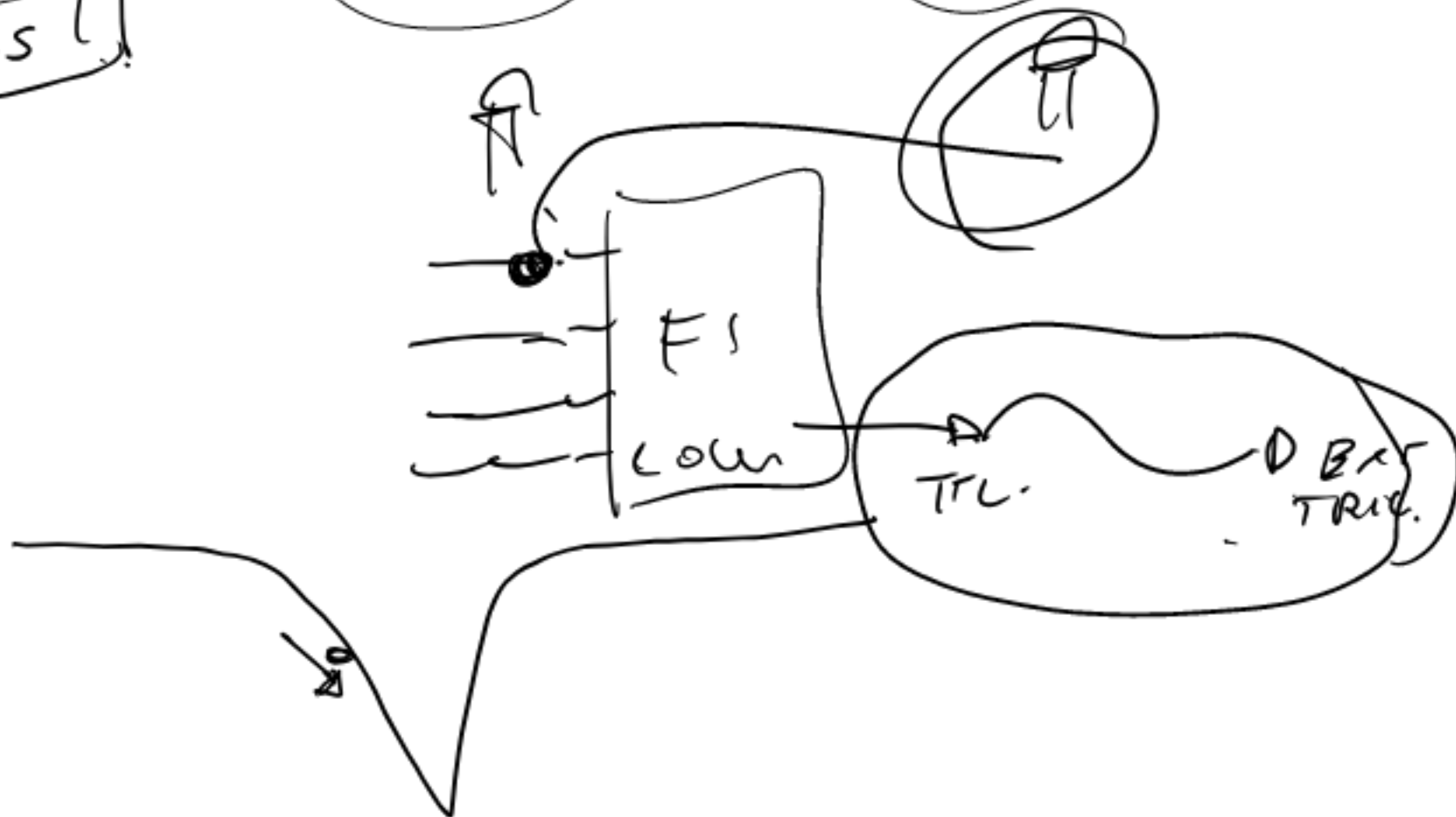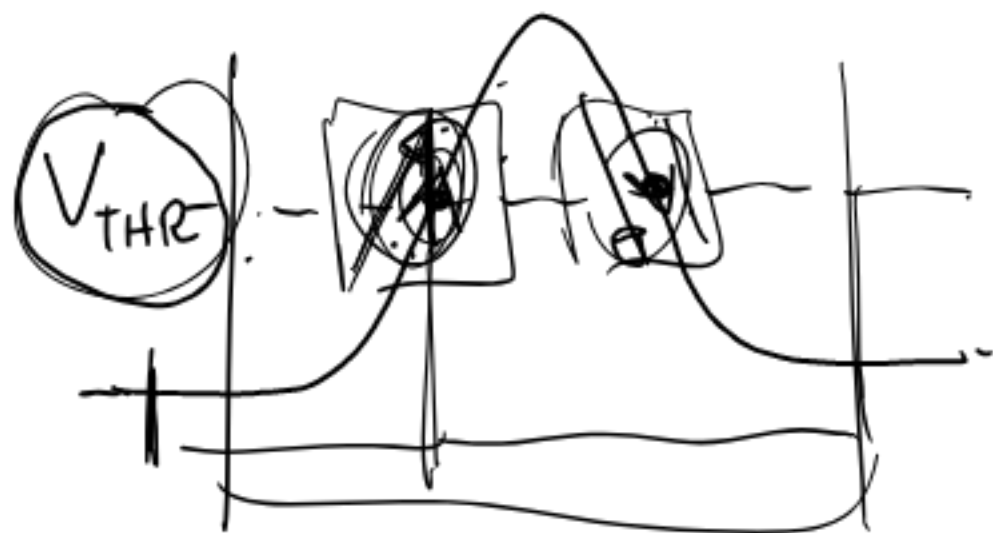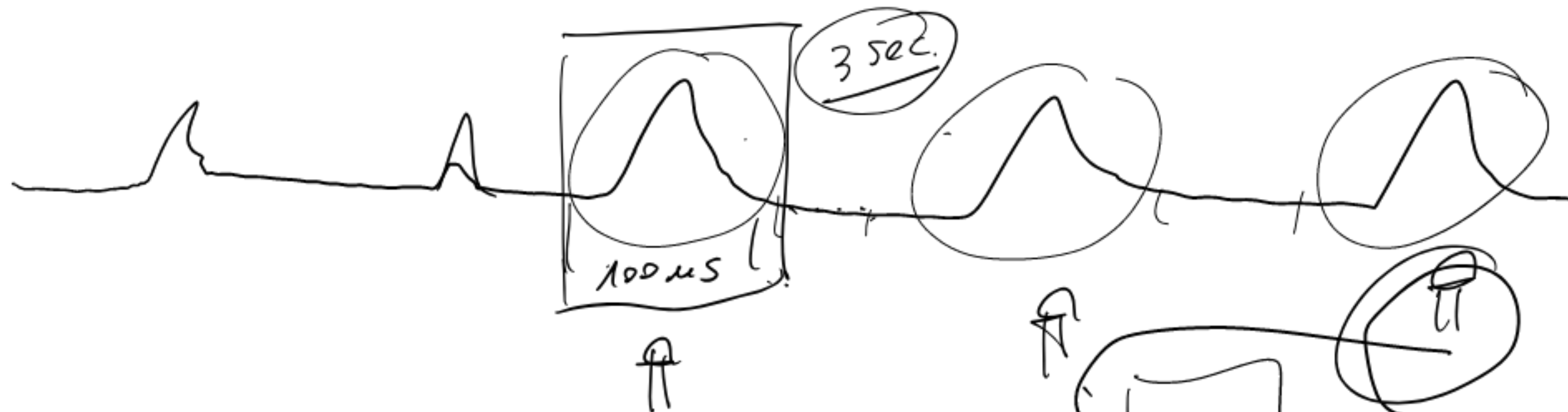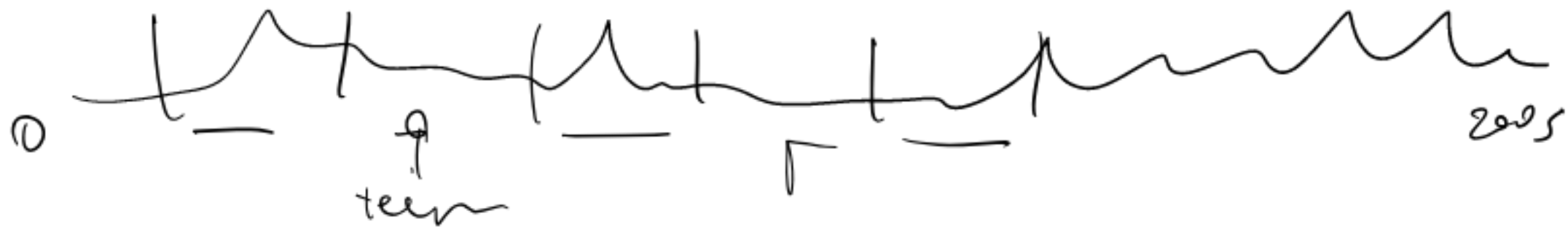

RAGGI COSMICI

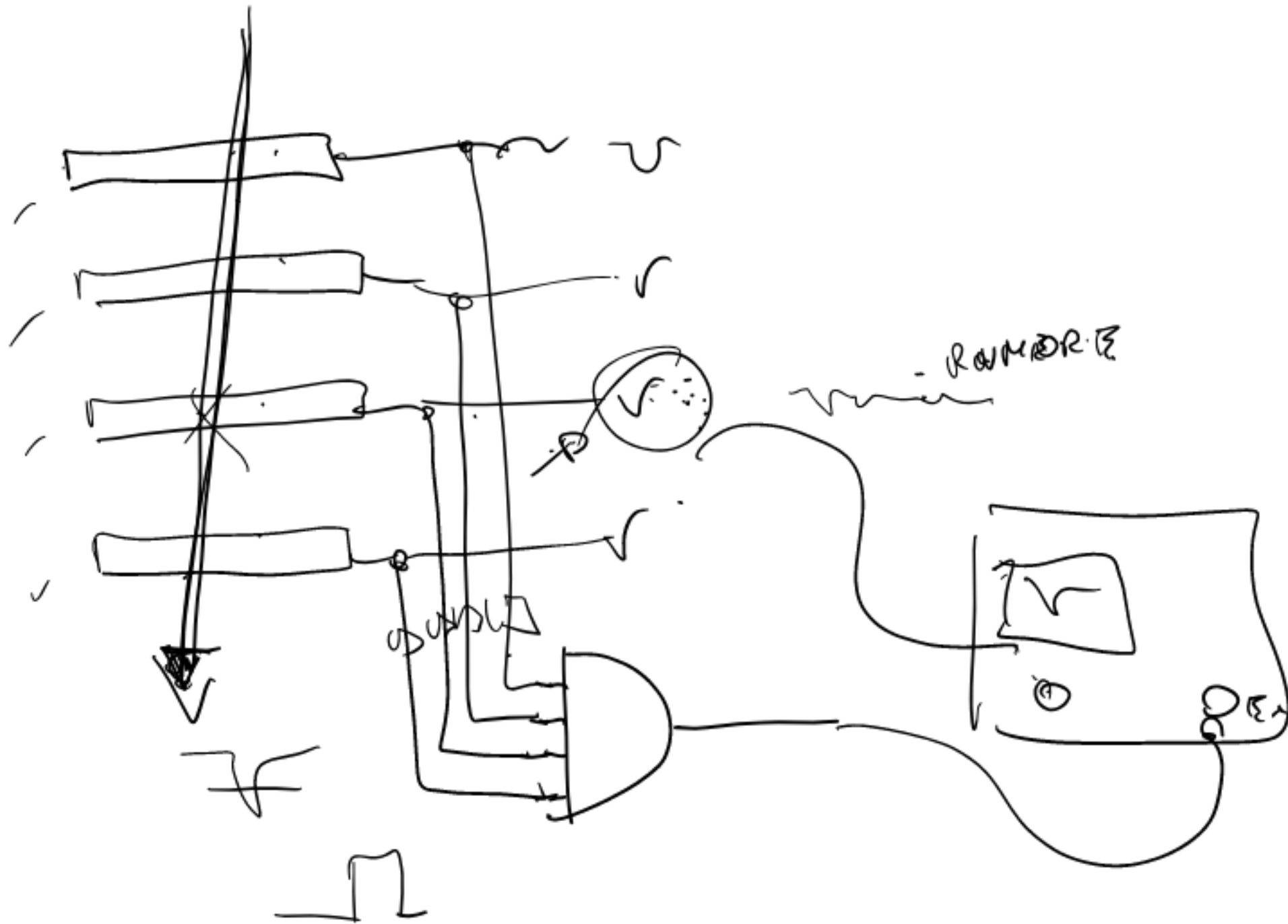


ESPERIENZE

ESP. 1
FILTRI


RC / ER

$T(f) = \frac{|V_{out}|}{|V_{in}|}$ RC-CR.

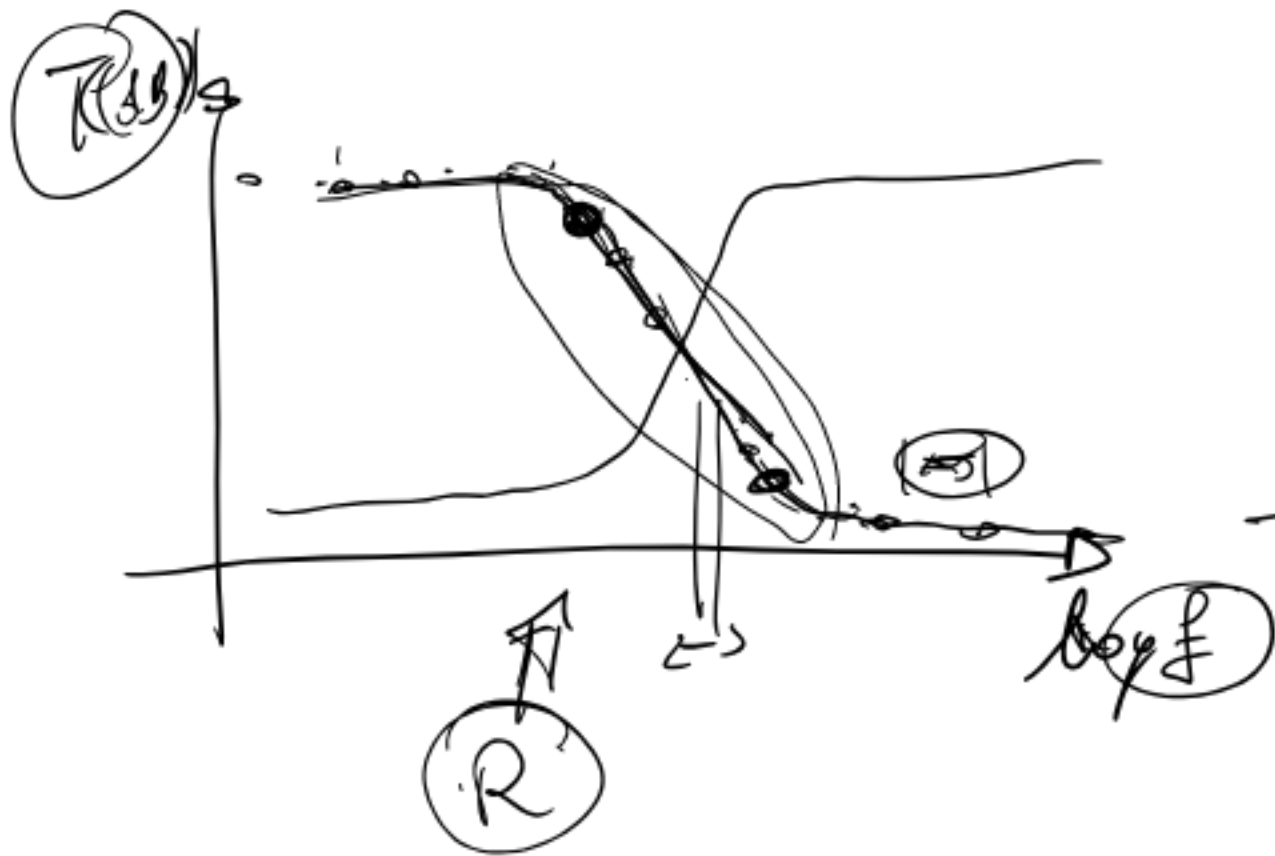

ESP. 2

PWM → Analogico $V \propto DC$

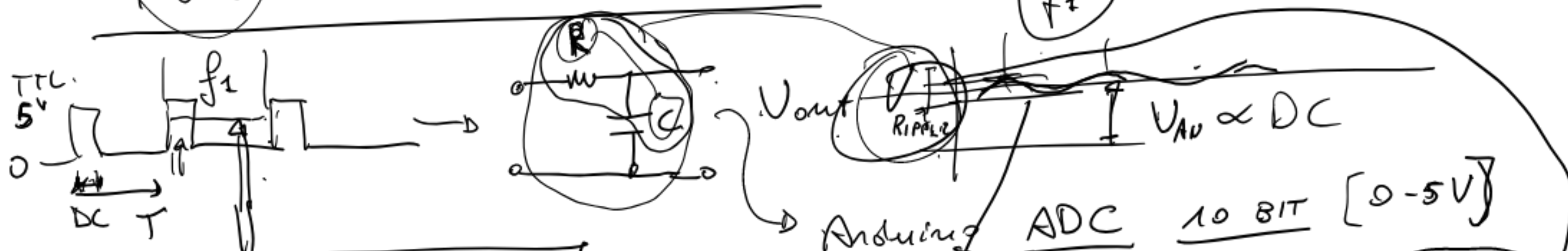

$f_{PWM} \approx 1 \text{ kHz}$

Analogico ADC 10 BIT [0-5V]
 $\frac{5V}{1023} \approx 5 \text{ mV}$

1 RC ⇒ $V_{RIPPLE} = 5 \text{ mV} / 1 \text{ mV}$



2 T RISPOSTA : $DC_1 \rightarrow DC_2$
 10% → 30% $\Delta T_{\alpha} = 0$
 $V_{out-1} \rightarrow V_{out-2}$
 $\Delta T_V = 999 \rightarrow RC$

3 3 volow V_{RIPPLE}
 $1 \text{ mV} / 10 \text{ mV} / 100 \text{ mV}$

ESP.1

DAC

4 BIT

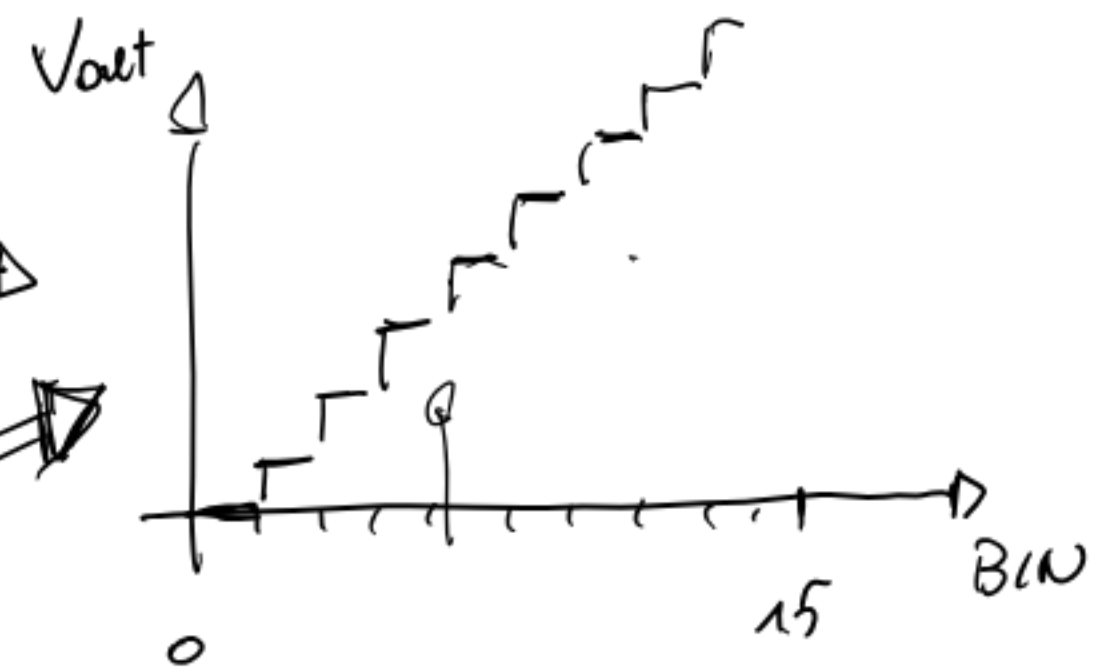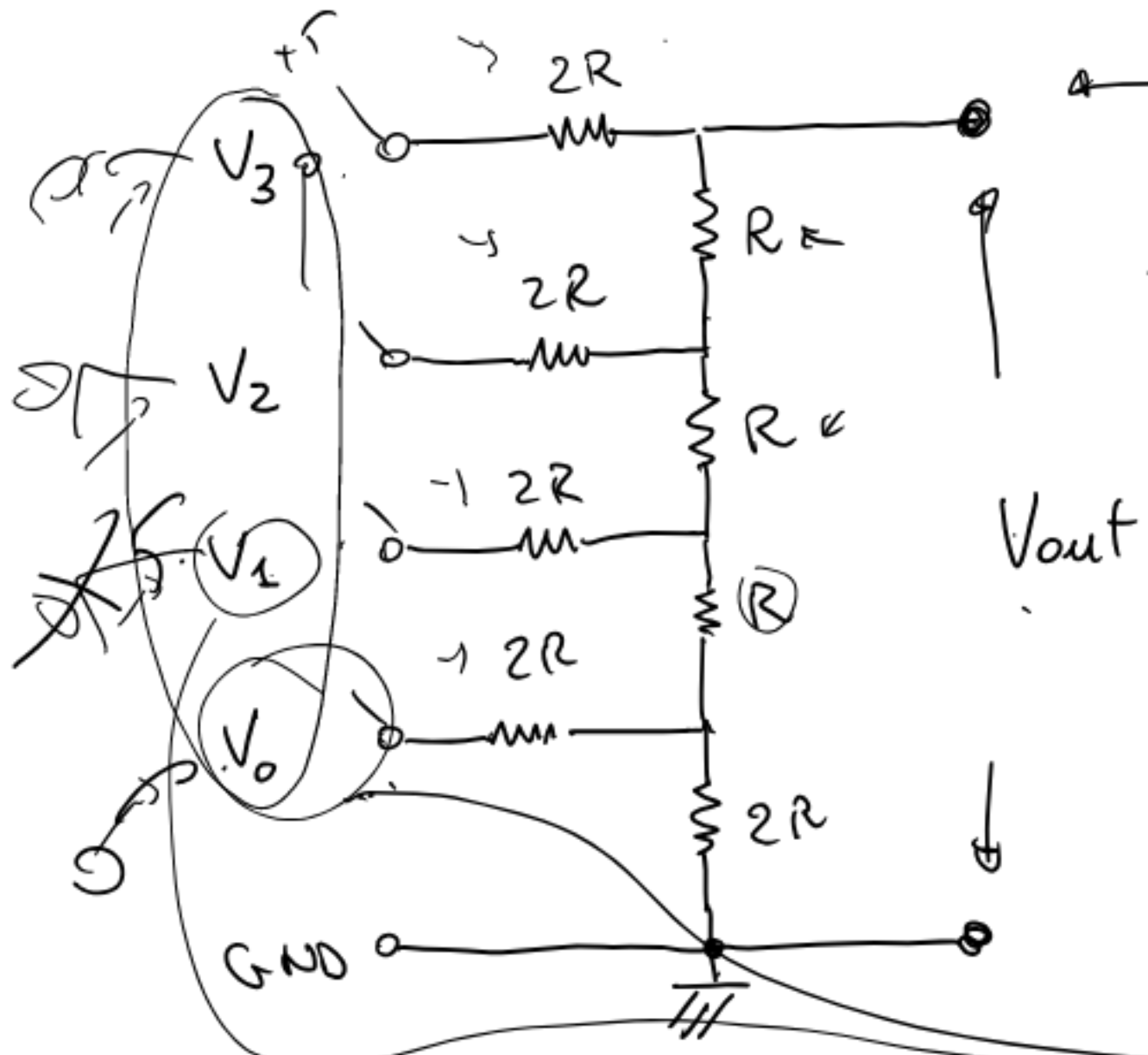

$$V_{out} = f(V_0, V_1, V_2, V_3)$$

???

~~$$V_{out} = V_0 \frac{R}{R} + V_1 \frac{R}{R} + V_2 \frac{R}{R} + V_3 \frac{R}{R}$$~~


$V_i = \begin{cases} 0 \rightarrow 10 \\ 1 \rightarrow 5V \end{cases}$

Vout ?



ESP.2

FILTRO

PBosco / Pass Alto / Pass Basso

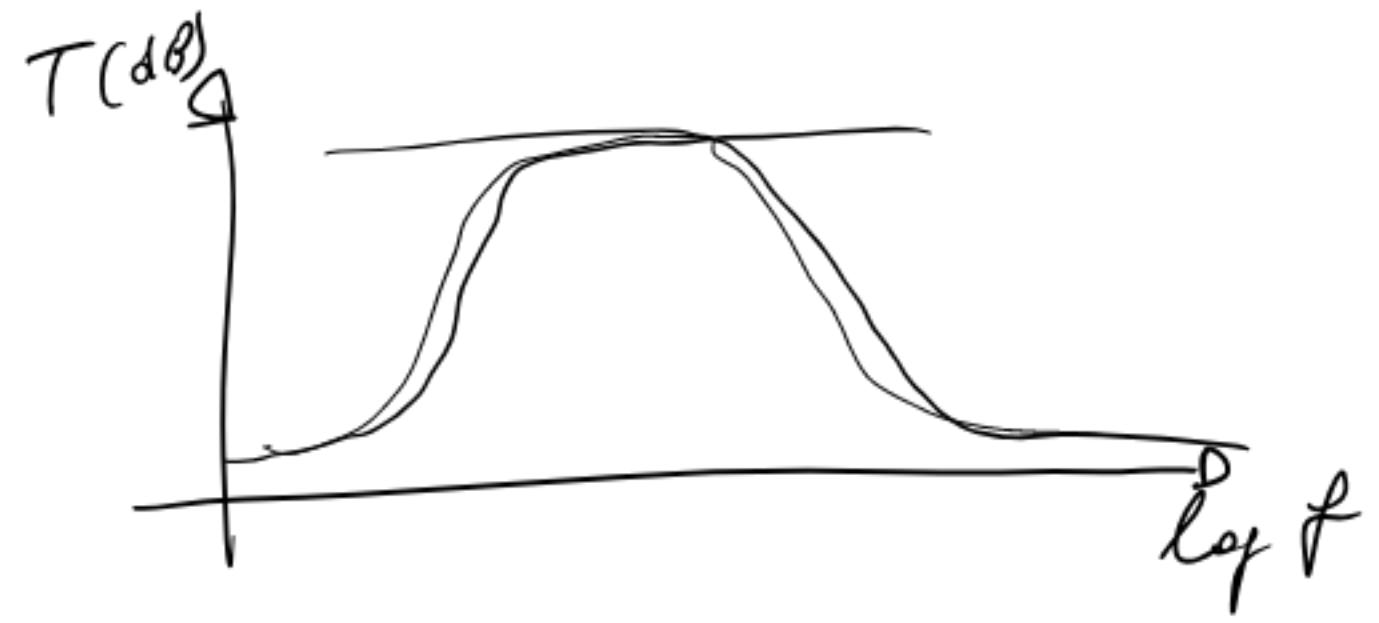

ESP.3

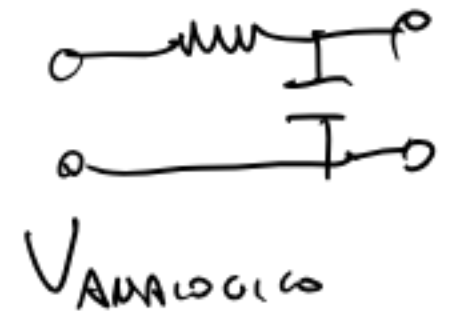
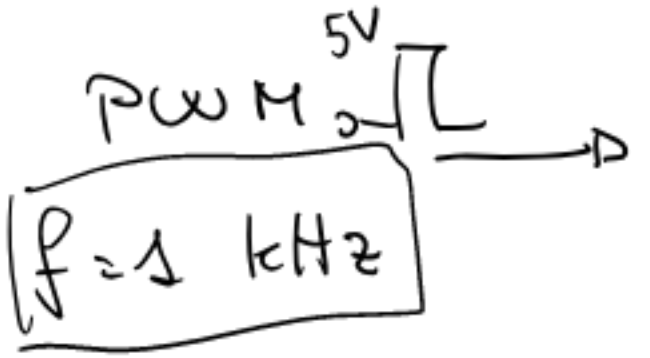


$V_{RIPPLE} = 1 \text{ mV}$
 $\frac{10 \text{ mV}}{100 \text{ mV}}$

Tworstage?

$DC_1 = 10\%$ \rightarrow $DC_2 = 90\%$
 $\Delta T = 0$

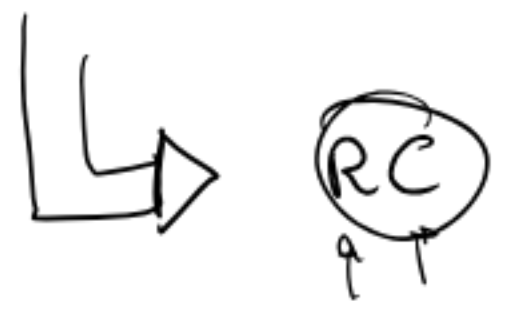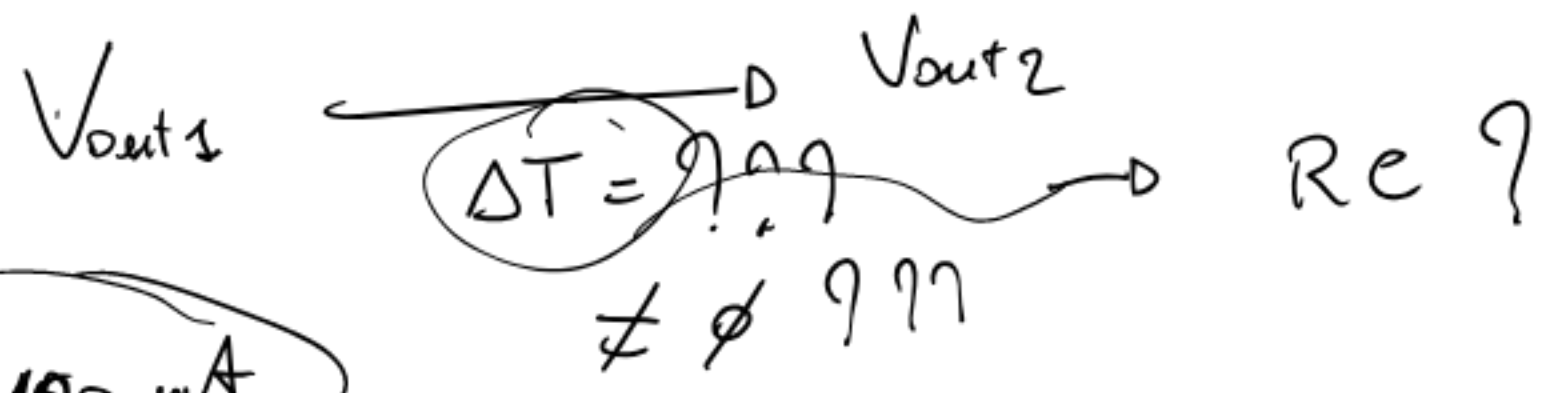$T(f = 1 \text{ kHz}) \Rightarrow 1 \text{ mV}$



$I = 100 \text{ uA}$